

## MODEL QUESTION

Level: Bachelor	Semester – Spring	Year : 2023
Programme: BESE, BECE		Full Marks: 100
Course: Digital Logic		Pass Marks: 45
First Year: First Semester		Time : 3hrs.

*Candidates are required to give their answers in their own words as far as practicable.*

*The figures in the margin indicate full marks.*

***Attempt all the questions.***

1. a) Explain how Digital and Analog electronic systems are different. Also list out the advantages of digital system. 5
- b) Perform the following operation using 9's complement and 2's complement method. 5
  - i)  $(743)_{10} - (234)_{10}$
  - ii)  $(234)_{10} - (743)_{10}$
- c) Convert the following numbers from the given base to the other bases indicated. 5
  - i)  $(11001.111)_2 = ( )_8$
  - ii)  $(5FE.DD)_{16} = ( )_8$
  - iii)  $(203)_8 = ( )_4$
  - iv)  $(777)_8 = ( )_{16}$
  - v)  $(1100)_{\text{GRAY CODE}} = ( )_2$
2. a) Simplify the following function F using don't care conditions d, in (1) sum of products and (2) product of sums using K-map 5
  - i)  $F = A'B'D' + A'CD + A'BC$   
 $d = A'BC'D + ACD + AB'D'$
- b) State and verify De-Morgan's theorem for two variables using truth table. 5
- c) Write down the differences between combinational logic and sequential logic. 5

3. a) Use Boolean theorems and postulates to simplify the following function and realize the simplified form using NAND gates only. 7

$$F = AB + A'C + BC$$

- b) Design a code converter circuit which converts 3 bit Code to GRAY CODE and draw the logic diagram. 8

OR

Design a 3 bit odd parity generator and 4 bit parity checker using exclusive gates.

4. a) What do you mean by DE-Multiplexer? Implement the following Boolean function  $F(w, x, y, z) = \sum_m(1, 2, 5, 7, 11, 15)$  using 8 to 1 Multiplexer with w, x, y as selection lines  $S_2, S_1$  and  $S_0$  respectively. 4

- b) Implement the following functions using ROM. 4

$$F_1(X, Y) = \sum(0, 2, 3)$$

$$F_2(X, Y) = \sum(1, 2)$$

- c) A combinational circuit is defined by the function 7

$$F_1(X, Y) = XY' + XZ \text{ and } F_2(X, Y) = XZ + YZ$$

Implement the circuit with a PLA having three inputs, three product terms and two outputs.

5. a) Explain JK Flip with its logic diagram, truth table and characteristics equation. 5

- b) Use 'D' flip-flop to design a 3-bit Synchronous UP Counter. 5

- c) Convert the JK Flip flop to realize D Flip flop. 5

6. a) A sequential circuit with two D Flip flops, A and B; two inputs, x and y; and one output, z, is specified by the next state and output equations: 8

$$A(t+1) = x'y + xA$$

$$B(t+1) = x'B + xA$$

$$\text{and } z = B$$


- i) Draw Logic diagram of the circuit. 7

- ii) Derive state table

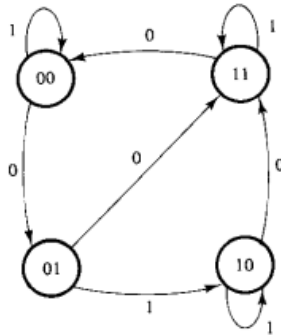iii) Draw state diagram

OR

Draw the sequential circuit from the information provided in the state diagram in the figure below using D flip-flops.



b) Design a 4-bit arithmetic circuits which performs eight different arithmetic operations.

7. Write short notes on: (**Any Two**)

2×5

- a) Output Hazard
- b) RAM
- c) Shift Register